



ECE 342 Optical Link Project

LAB 4: LED DRIVER

Function in the Optical Link Project




- ▶ The second stage in the transmitter transmits an optical signal that is modulated at the clock frequency provided by the signal generator stage
- ▶ An LED driver sources a specified amount of current to an LED
 - ▶ LED light output is a function of the drive current (approximately linear)
 - ▶ The LED driver can modulate the current as a function of the input
 - ▶ In this case, the LED driver will turn the LED on and off at a rate of 20 kHz
- ▶ A signal conditioning circuit may be necessary to modify the signal generator output to a 50% duty cycle rail-to-rail square wave

Task Objectives

- ▶ Design, construct and test an LED driver that sources a 50% duty-cycle 40 mA peak current square wave to the IR LED
- ▶ Design, construct and test a signal conditioning circuit that will convert the output of the 3-stage ring oscillator circuit to an approximately 50% duty cycle square wave


IR1503 LED Characteristics

I-V Characteristics

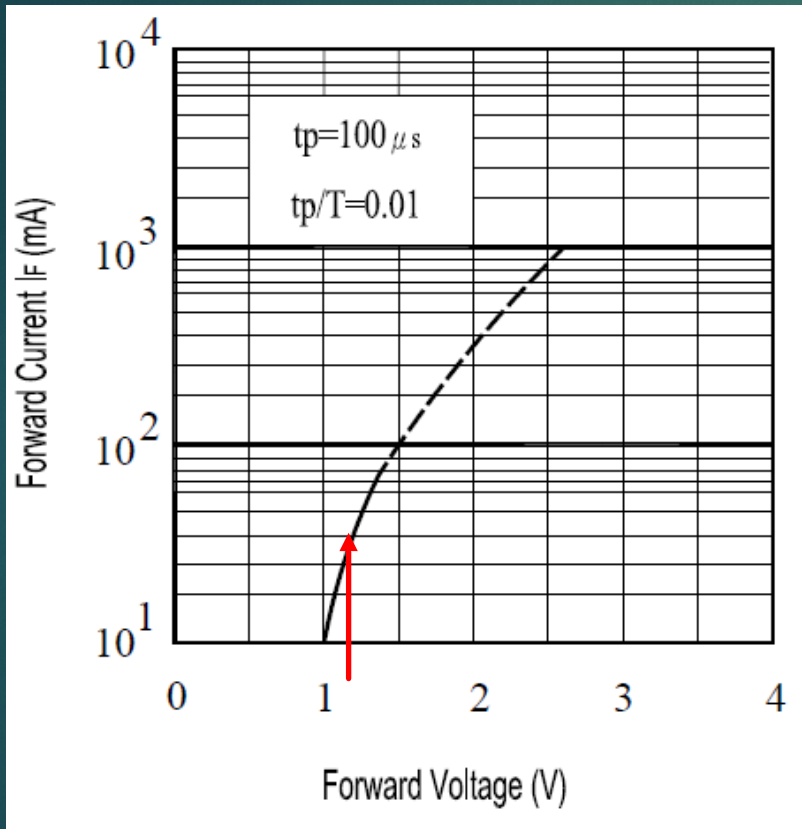

$V_F \cong 1.2 \text{ V}$ for $I_F = 40 \text{ mA}$

Radiant Intensity vs. Forward Current

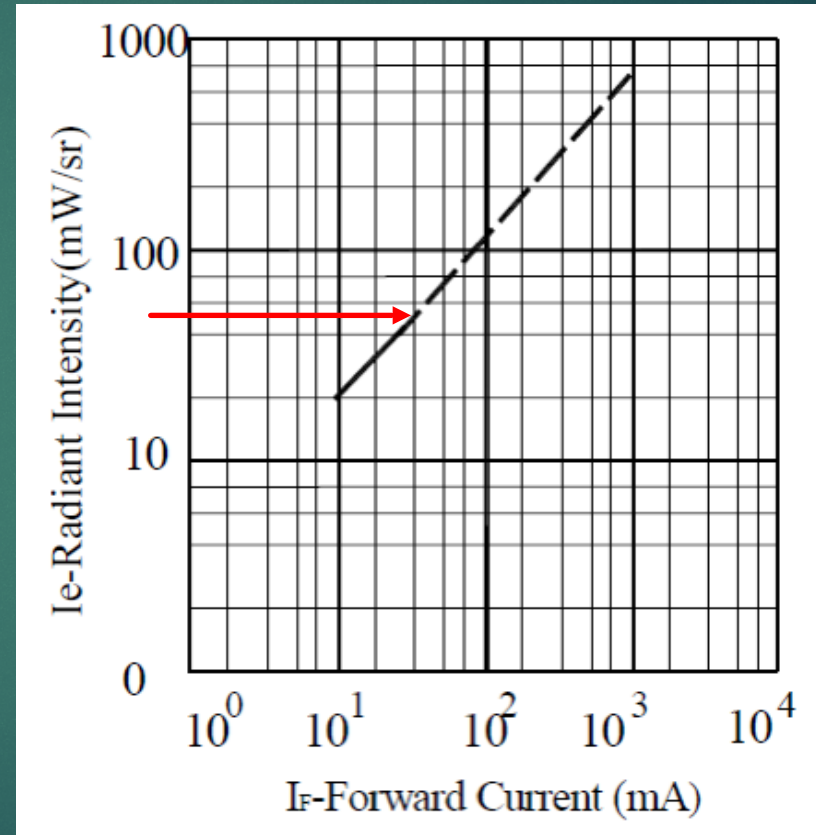

Radiant intensity $\cong 50 \text{ mW/sr}$ for $I_F = 40 \text{ mA}$

LED Driver – Basic Principle

- ▶ The LED driver uses an op-amp transconductance circuit

- ▶ Input is voltage
- ▶ Output is current


- ▶ The current through the LED is:

$$I_{LED} = \frac{V_{control}}{R_{sense}}$$

- ▶ The op-amp output voltage swing must be able to support the voltages across the LED and sense resistor


- ▶ The supply voltage $V_{CC} > V_{control} + V_{LED}$

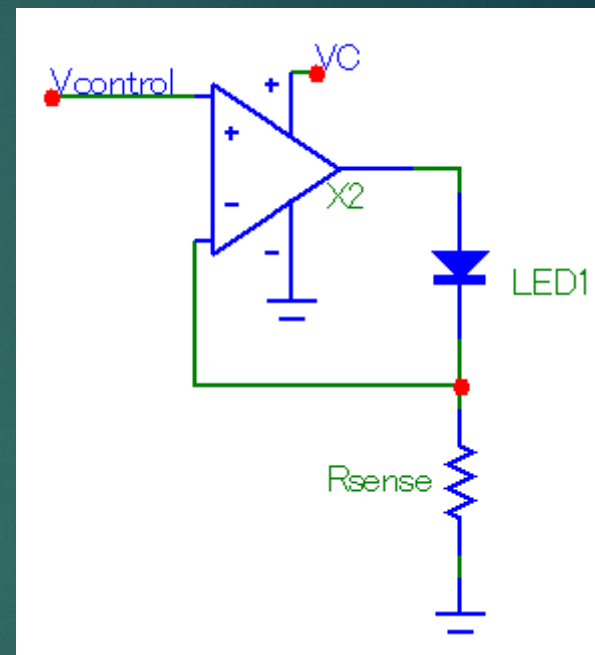- ▶ The op-amp must be able to supply the LED current
 - ▶ Most op-amps can source 20-30 mA



LED Driver for Higher Current

- ▶ Use a bipolar junction transistor (BJT) to source higher amounts of current
 - ▶ The op-amp only needs to source 1/10th to 1/100th of the LED current
 - ▶ Output voltage swing must include the base-emitter voltage drop V_{BE}
 - ▶ V_{BE} is usually ~ 0.7 V
- ▶ The resistive voltage divider R1-R2 lowers $V_{control}$
 - ▶ $V_{control}$ is 0 V to 5 V
 - ▶ Op-amp supply is 5 V
 - ▶ Voltage at V_- needs to be at least 2 V below supply, to accommodate $V_{BE} + V_{LED1}$

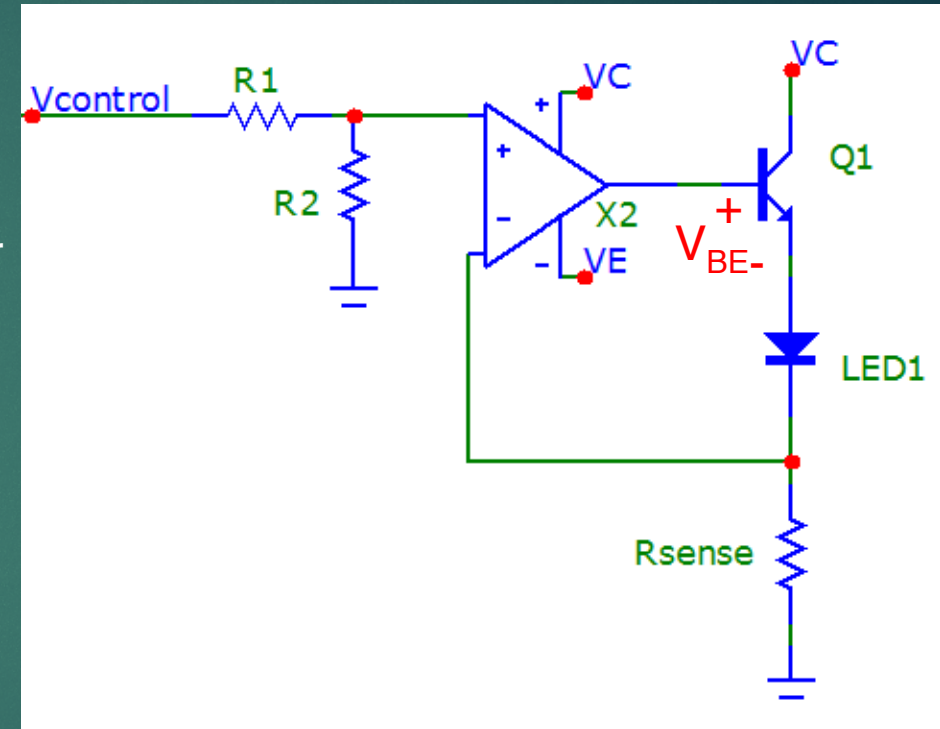

The Bipolar Junction Transistor (BJT)

- ▶ A three terminal device which can be used as a current amplifier
 - ▶ Base (B)
 - ▶ Collector (C)
 - ▶ Emitter (E)


- ▶ The collector current is an amplified version of the base current

$$I_C = \beta I_B$$

- ▶ True only for the forward active mode
- ▶ The emitter current is the sum of the two


$$I_E = I_B + I_C$$

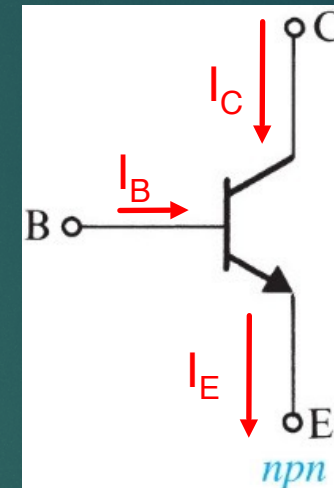- ▶ Will study BJTs in Chapter 6
- ▶ See Chapter 6 pre-lecture videos 1 and 2 for more information on device structure, operation principle and I-V characteristics





Signal Conditioning Circuit

- ▶ The output of the digital oscillator may not be a 50% duty cycle square wave
 - ▶ Ring oscillator output probably not 0 V to 5 V
- ▶ Need a signal conditioning circuit
 - ▶ Analog voltage comparator (e.g. LM319)
 - ▶ Op-amp based voltage amplifier
- ▶ The MCP6004 has four op-amps
 - ▶ One will be used for the LED driver
 - ▶ Three more op-amps available
- ▶ Potentiometer used to adjust V_{ref} to obtain a 50% duty cycle square wave
- ▶ The PSRR of the shown circuit is only 6 dB
 - ▶ Can this be improved?

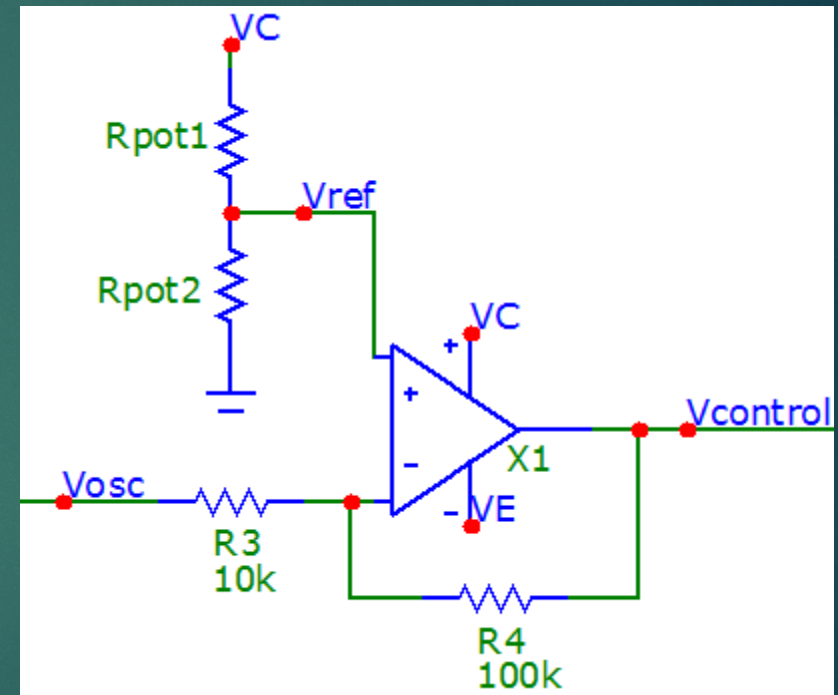

Linear Voltage Regulator

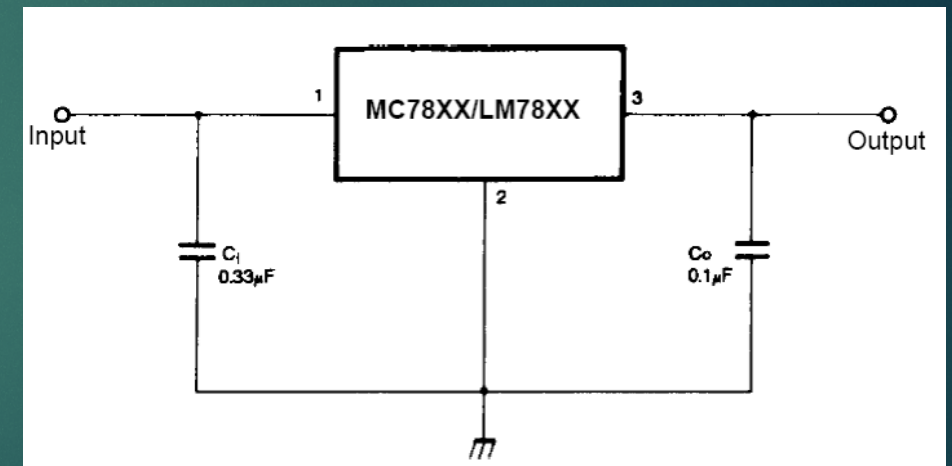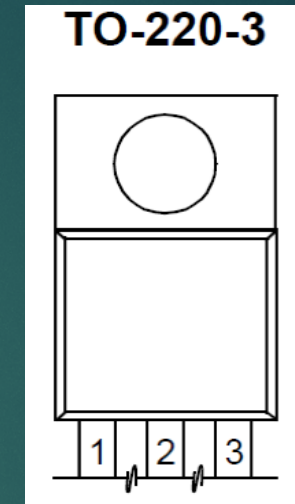- ▶ Transmitter circuit will be powered by a 9 V battery
 - ▶ Use a power supply for this Task
- ▶ LM7805 +5 V linear voltage regulator
 - ▶ Regulates the supply voltage down to +5 V
 - ▶ Will drop $9\text{ V} - 5\text{ V} = 4\text{ V}$
- ▶ TO-220-3 package with
 - ▶ Pin 1: Input
 - ▶ Pin 2: GND
 - ▶ Pin 3: Output
 - ▶ Backside metal: GND
- ▶ Smoothing capacitors at input and output



Tasks

- ▶ Design LED driver to deliver 40 mA peak current to LED
 - ▶ Calculate the values for R1, R2, and Rsense, assuming 0 V to 5 V input
- ▶ Design the signal conditioning circuit
- ▶ Simulate the full transmitter circuit
- ▶ Construct and test the full transmitter
 - ▶ Ensure LED drive current is 40 mA peak 50% duty cycle square wave

Tips and Tricks

- ▶ This lab should be straightforward and quick to do
- ▶ Measure voltage across R_{sense} to determine the LED drive current
- ▶ An alternative LED driver places the LED between the BJT's collector and the battery
- ▶ If a signal conditioning circuit is required, make sure the PSRR at 20 kHz is at least 60 dB

