 


## Solving the Output Voltage of a Resistively Loaded MOSFET Logic Gate

### A. Solving the Output Voltages for Logic 0 and Logic 1 Inputs



The figure above shows a resistively loaded NMOS inverter logic gate, constructed with an enhancement mode MOSFET, as used in Task 3. There are two extremes that need to be considered for logic operations:

- Logic 0 input:  $V_{\text{gate}} = 0 \text{ V}$ , and the logic 1 output will be  $V_{\text{drain}} = V_{\text{DD}}$ .
- Logic 1 input:  $V_{\text{gate}} = V_{\text{DD}}$ , and the logic 0 output will be  $V_{\text{drain}} = 0 \text{ V}$ .

The first, logic 0 input / logic 1 output, corresponds to no current flowing through the circuit, and the MOSFET is operating in cut-off, i.e. it is off.

$$\text{Cut-off: } |V_{\text{GS}}| < |V_{\text{t}}| \quad I_{\text{DS}} = 0$$

The second, logic 1 input / logic 0, corresponds to the MOSFET operating in the triode regions, as  $V_{\text{gate}} = V_{\text{DD}}$  but  $V_{\text{drain}} \approx 0 \text{ V}$ , therefore  $V_{\text{DS}} < V_{\text{GS}} - V_{\text{t}}$ . For an NMOS, this gives:

$$\text{Triode: } |V_{\text{GS}}| < |V_{\text{t}}| \text{ and } |V_{\text{DS}}| < |V_{\text{GS}} - V_{\text{t}}|$$

$$I_{\text{DS}} = \mu_n C_{\text{ox}} \frac{W}{L} \left[ (V_{\text{GS}} - V_{\text{t}}) V_{\text{DS}} - \frac{1}{2} V_{\text{DS}}^2 \right]$$

Calculating the output voltage for a logic 1 input requires solving two coupled equations. The current through the drain resistor,  $I_{\text{R}}$ , is equal to the drain current,  $I_{\text{DS}}$ , of the NMOS FET. The current across the resistor is:

$$I_{\text{R}} = \frac{V_{\text{DD}} - V_{\text{DS}}}{R_{\text{drain}}} \quad (\text{Eq. 1})$$

The drain current is:

$$I_{\text{DS}} = \mu_n C_{\text{ox}} \frac{W}{L} \left[ (V_{\text{GS}} - V_{\text{t}}) V_{\text{DS}} - \frac{1}{2} V_{\text{DS}}^2 \right] \quad (\text{Eq. 2})$$

Equating the two currents gives:

$$\frac{V_{DD} - V_{DS}}{R_{drain}} = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

Defining  $k = R_{drain} \mu_n C_{ox} \frac{W}{L}$ , we can re-write the equation as:

$$\frac{k}{2} V_{DS}^2 - \left[ k(V_{GS} - V_t) + 1 \right] V_{DS} + V_{DD} = 0 \quad (Eq. 3)$$

The two roots for an equation in the form of  $ax^2 + bx + c = 0$  are  $x_{1,2} = \frac{-b \pm \sqrt{\Delta}}{2a}$

where  $\Delta = b^2 - 4ac$ . Only one of the two roots will be physically meaningful and therefore the correct solution. To be meaningful, the correct root for  $V_{DS}$  should ensure the device is operating (i) within the supply voltage limits, and (ii) the MOSFET is operating in the triode region.

*Example 1. Solving for the logic 0 and logic 1 output levels*

As an example, let's assume  $V_{DD} = 5$  V,  $R_{drain} = 20$  k $\Omega$ , and that the NMOS FET has  $\mu_n C_{ox} \frac{W}{L} = 1 \frac{mA}{V^2}$  and  $V_{t,n} = 1$  V.

- The output for Logic 0 input, i.e. Logic 1 output is  $V_{out} = V_{drain} = V_{DD} = 5$  V.
- What about the output for Logic 1 input? We can either use equation (3), or solve the two equations explicitly.

The current across the resistor is:

$$I_R = \frac{V_{DD} - V_{DS}}{R_{drain}} = \frac{5 - V_{DS}}{20,000}$$

The drain current is:

$$I_{DS} = \mu_n C_{ox} \frac{W}{L} \left[ (V_{GS} - V_t) V_{DS} - \frac{1}{2} V_{DS}^2 \right] = 1 \times 10^{-3} \times \left[ (5 - 1) V_{DS} - 0.5 V_{DS}^2 \right]$$

$$I_{DS} = 10^{-3} \times [4V_{DS} - 0.5V_{DS}^2]$$

So when we equate the two:

$$\frac{5 - V_{DS}}{20,000} = 10^{-3} \times [4V_{DS} - 0.5V_{DS}^2]$$

$$5 - V_{DS} = 20 \times [4V_{DS} - 0.5V_{DS}^2]$$

Hence, we will obtain:

$$10V_{DS}^2 - 81V_{DS} + 5 = 0$$

Solving for the roots give:  $V_{DS1} = 8$  V and  $V_{DS2} = 62$  mV.

The first root is not physically meaningful, as (i) it is larger than the supply voltage, and

(ii) would result in  $V_{DS} > V_{GS} - V_t$ , i.e. operation in the saturation mode instead of the in triode mode.

The physically meaningful root is  $V_{\text{drain}} = V_{DS2} = 62 \text{ mV}$ .

So a logic 0 output for this circuit is 62 mV.

#### B. Solving for an Arbitrary Input & Output Voltage Combination

One of the design sub-tasks in Task 3 is to determine the drain resistor value that will result in  $V_{\text{out}} = 2.5 \text{ V}$  when  $V_{\text{in}} = 2.5$ . To proceed with the solution, we need to determine if the MOSFET is operating in triode or saturation. Realizing that  $V_{\text{out}} = V_{DS}$  and  $V_{\text{IN}} = V_{GS}$ , we have:

- $V_{GS} = 2.5 \text{ V} > V_t = 1 \text{ V}$ , so the MOSFET is on, operating either in triode or saturation.
- $V_{DS} = 2.5 \text{ V} > V_{GS} - V_t = 1.5 \text{ V}$ . So the MOSFET is operating in saturation.

The MOSFET I-V characteristic for operation in saturation is:

$$I_{DS} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right) (V_{GS} - V_t)^2 \quad (\text{Eq. 4})$$

A more accurate version of this equation that accounts for the channel length effect includes a  $V_{DS}$  term as well. We will ignore that additional term for now.

Plugging in the parameters, we obtain:

$$I_{DS} = 0.5 \times 1 \text{ mA/V}^2 \times (2.5 - 1)^2 = 1.125 \text{ mA}$$

The resistor can be solved using:

$$R_{\text{drain}} = \frac{V_{DD} - V_{DS}}{I_R} = \frac{5 - 2.5}{1.125 \text{ mA}} = 2222 \Omega$$

Using the 5% tolerance resistor available in the parts store, we would choose  $R_{\text{drain}} = 2.2 \text{ k}\Omega$ .

For the CD4007UBE NMOS FET used in Task 3:

$$\mu_n C_{ox} \left( \frac{W}{L} \right) \cong 500 \frac{\mu A}{V^2}$$

$$V_{tn} = 0.95 \text{ V} \cong 1 \text{ V}$$